


BASIC PRINCIPLES
OF
COMMUNICATION
CIRCUITS

Circuit Definitions

- **Node** – any point where 2 or more circuit elements are connected together
 - Wires usually have negligible resistance
 - Each node has one voltage (w.r.t. ground)
- **Branch (rama)** – a circuit element between two nodes
- **Loop (lazo)** – a collection of branches that form a closed path returning to the same node without going through any other nodes or branches twice

Example


- How many nodes, branches & loops?

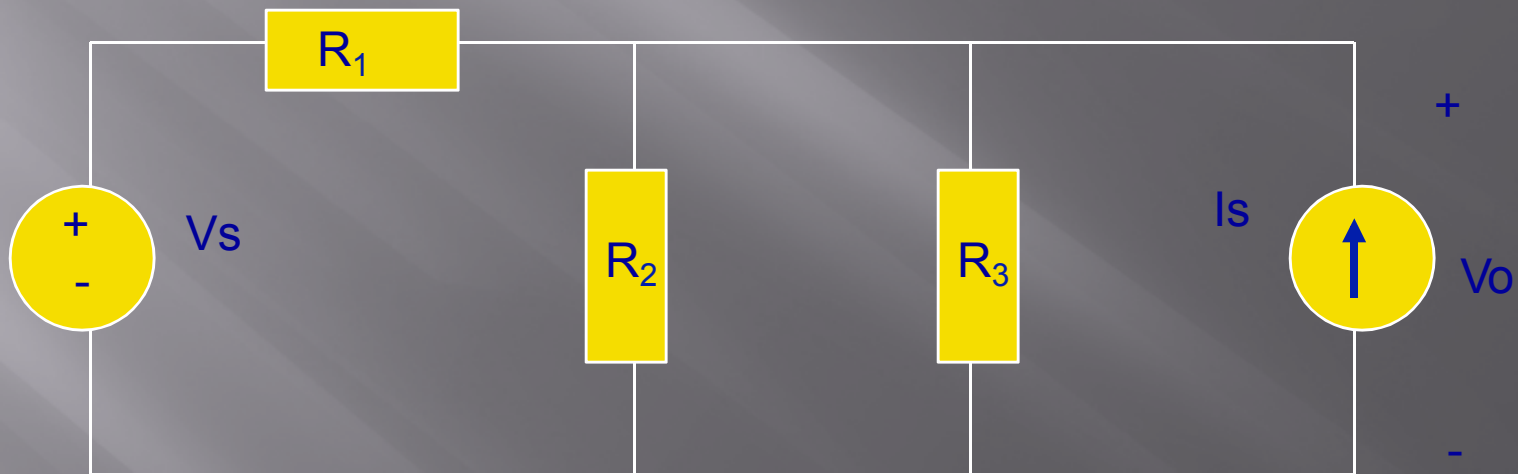

Example




Three nodes

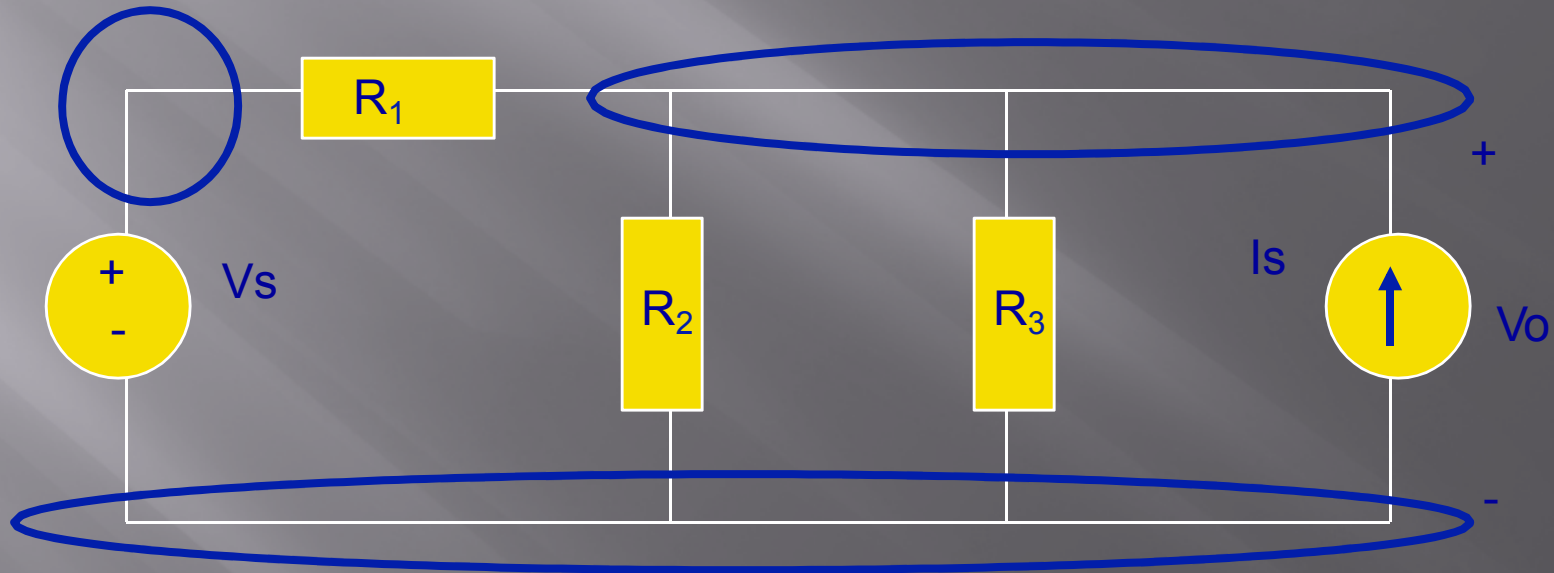


Example

 **5 Branches**

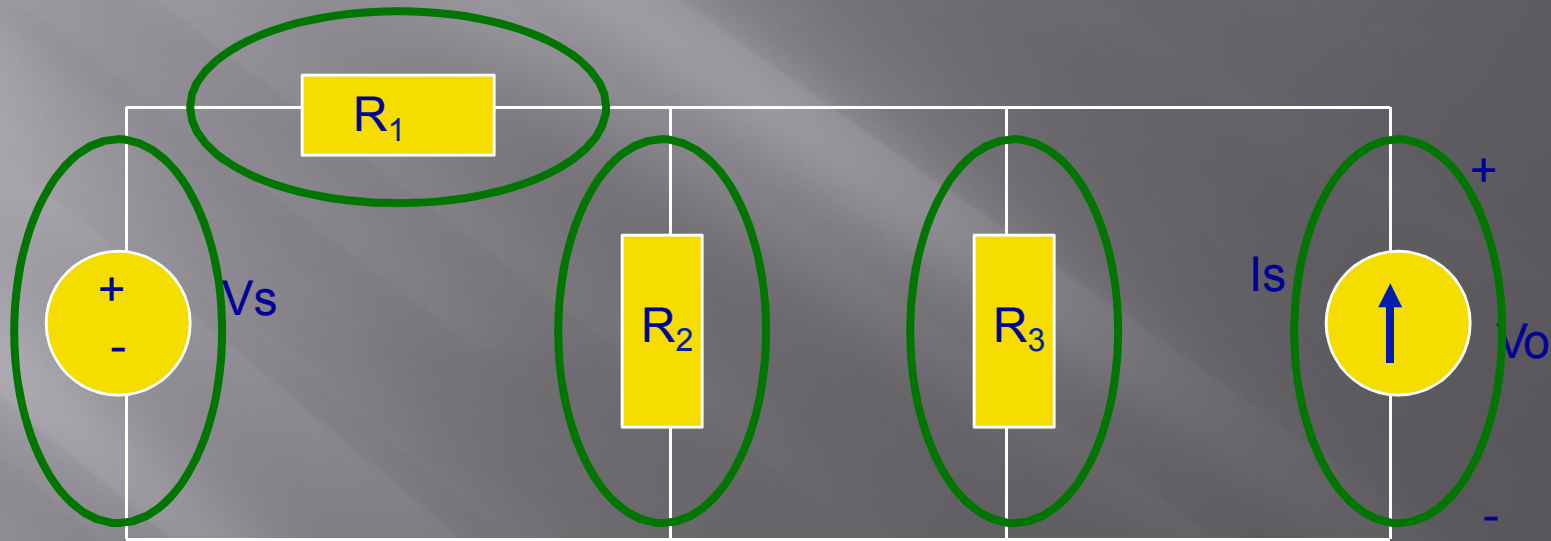

Example

- Three Loops, if starting at node A

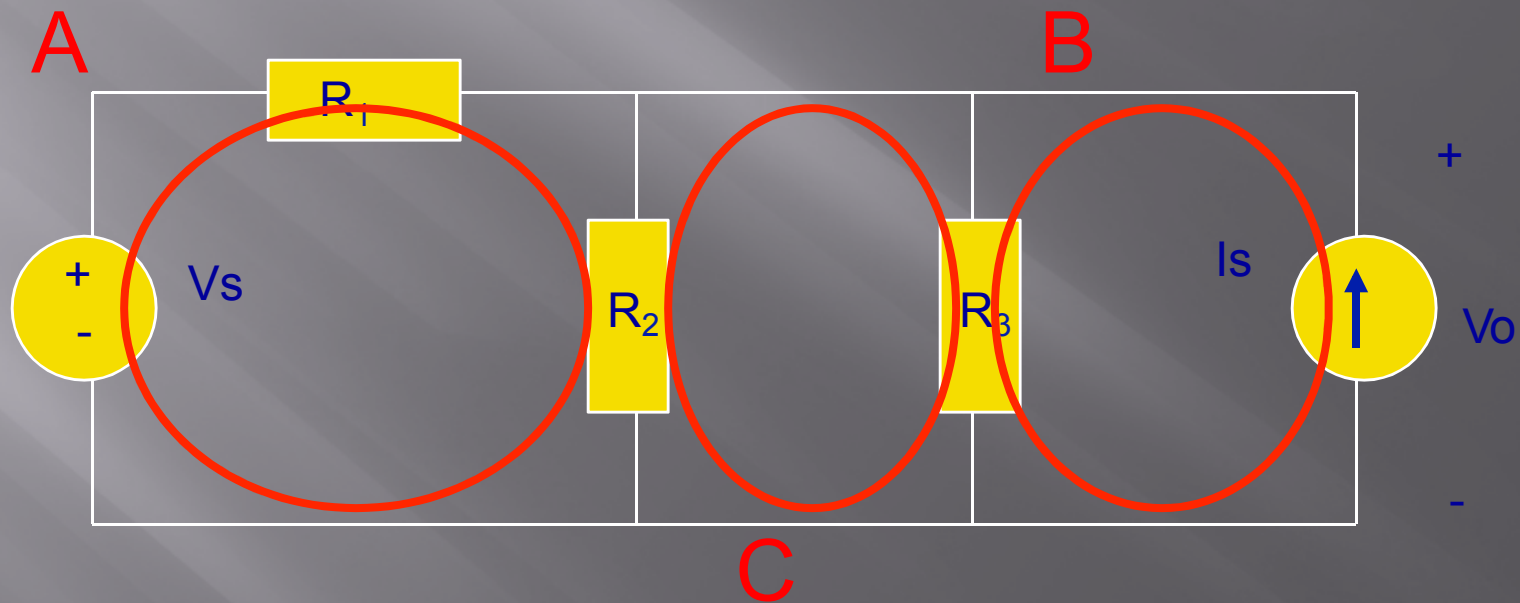


Kirchoff's Voltage Law (KVL)

- The algebraic sum of voltages around each loop is zero
- Beginning with one node, add voltages across each branch in the loop (if you encounter a + sign first) and subtract voltages (if you encounter a – sign first)
- Σ voltage drops - Σ voltage rises = 0
- Or Σ voltage drops = Σ voltage rises

Example

Kirchoff's Voltage Law around 1st Loop

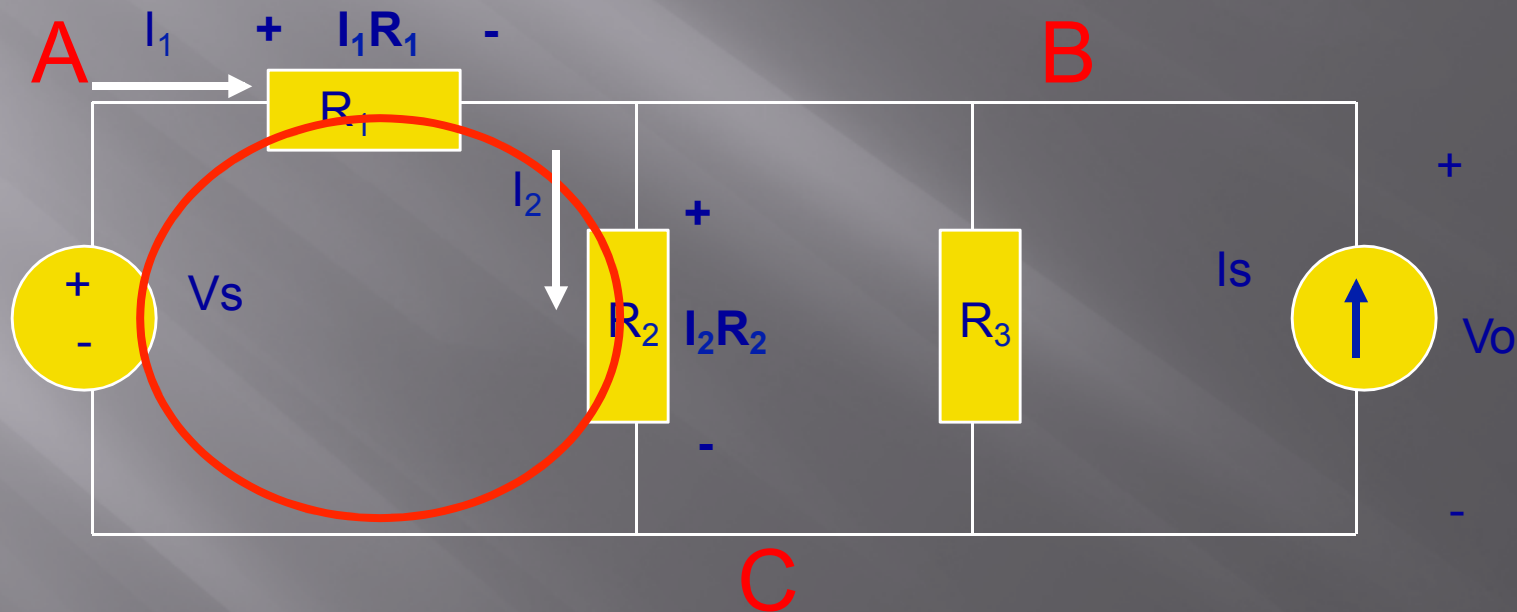


Assign current variables and directions

Use Ohm's law to assign voltages and polarities consistent with passive devices (current enters at the + side)

Example


Kirchoff's Voltage Law around 1st Loop

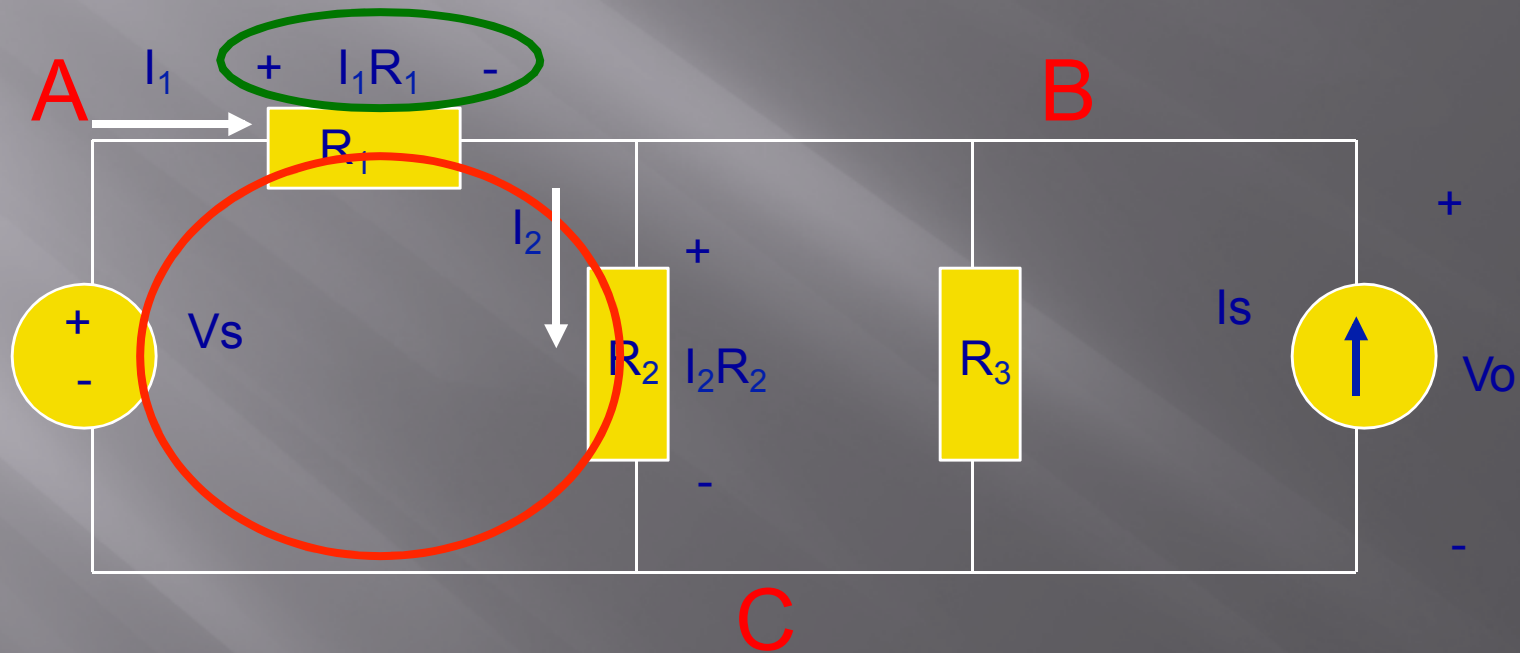

Starting at node A, add the 1st voltage drop: $+ I_1 R_1$

Example


Kirchoff's Voltage Law around 1st Loop

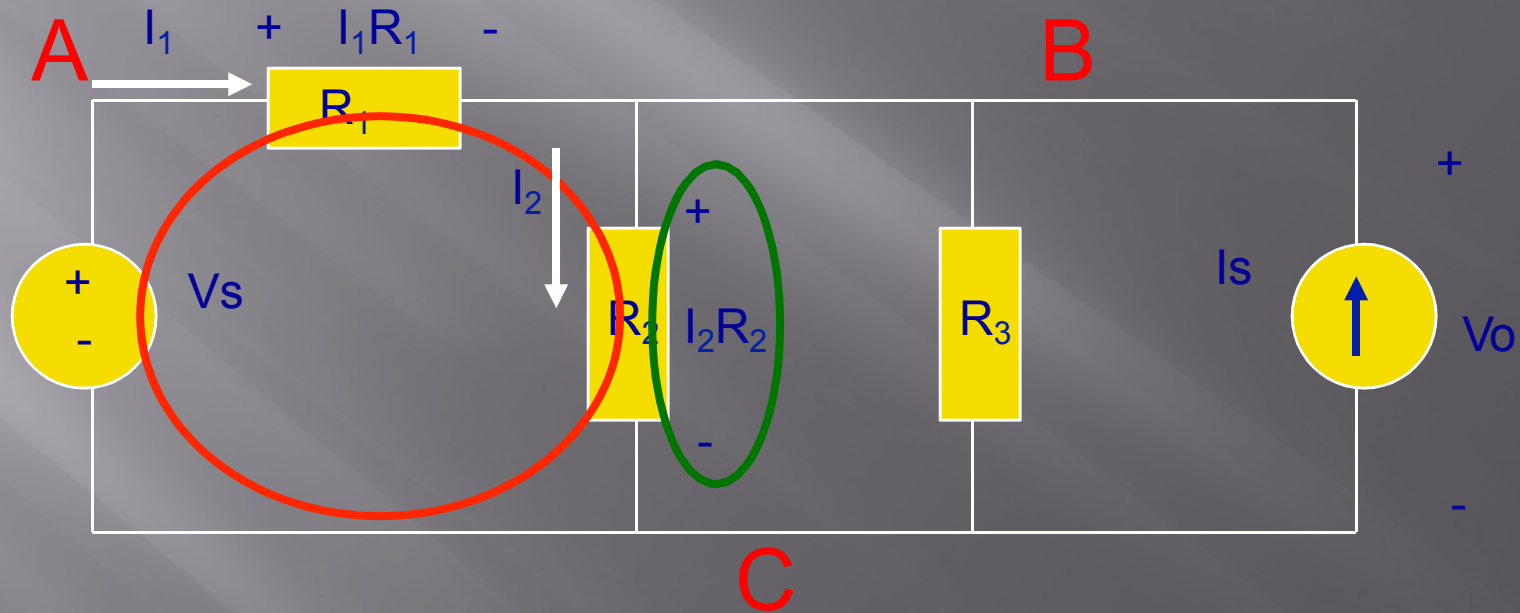

Add the voltage drop from B to C through R_2 : $+ I_1 R_1 + I_2 R_2$

Example

Kirchoff's Voltage Law around 1st Loop

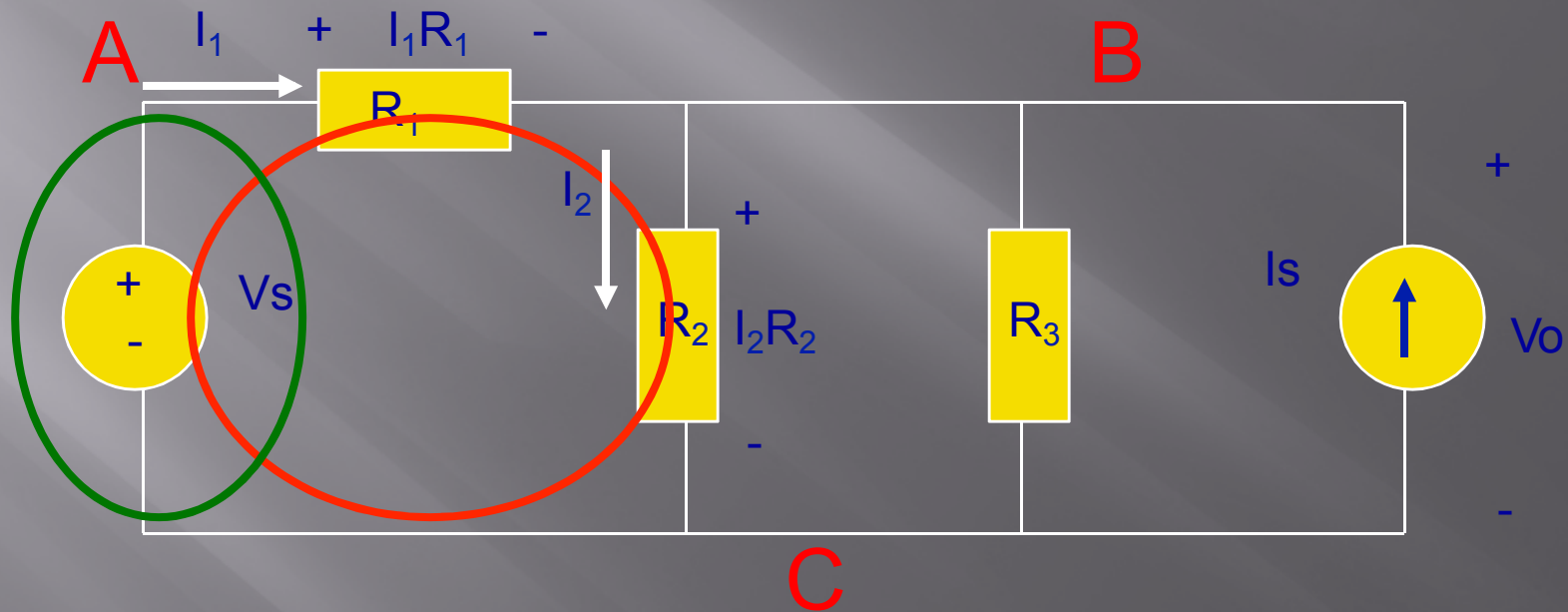


Subtract the voltage rise from C to A through V_s : $+ I_1 R_1 + I_2 R_2 - V_s = 0$

Notice that the sign of each term matches the polarity encountered 1st

Circuit Analysis

Circuit Analysis

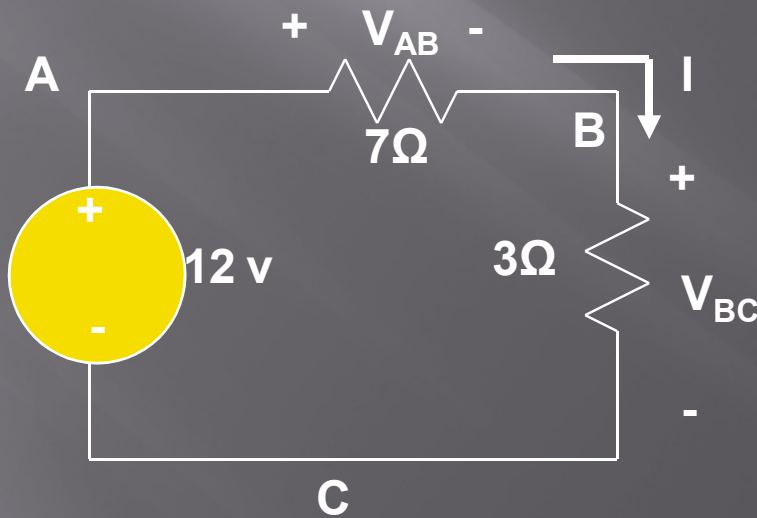- When given a circuit with sources and resistors having fixed values, you can use Kirchoff's two laws and Ohm's law to determine all branch voltages and currents




Circuit Analysis

By Ohm's law: $V_{AB} = I \cdot 7\Omega$ and $V_{BC} = I \cdot 3\Omega$

By KVL: $V_{AB} + V_{BC} - 12\text{ v} = 0$

Substituting: $I \cdot 7\Omega + I \cdot 3\Omega - 12\text{ v} = 0$

Solving: $I = 1.2\text{ A}$

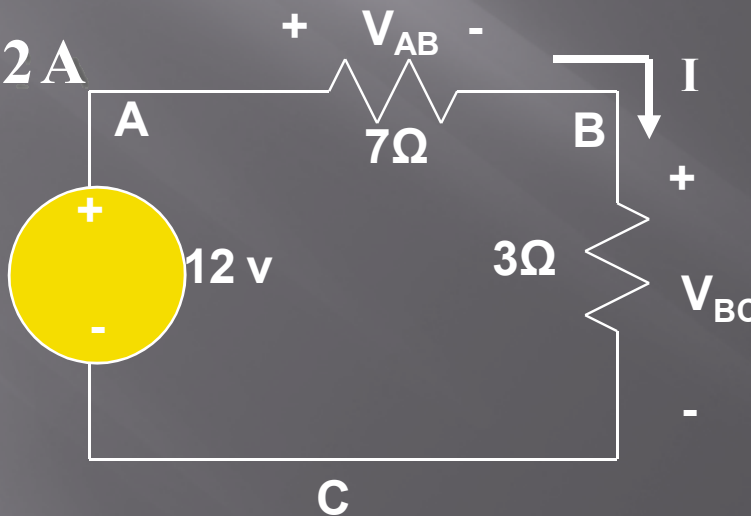


Circuit Analysis

Circuit Analysis

Since $V_{AB} = I \cdot 7\Omega$ and $V_{BC} = I \cdot 3\Omega$

And $I = 1.2 \text{ A}$

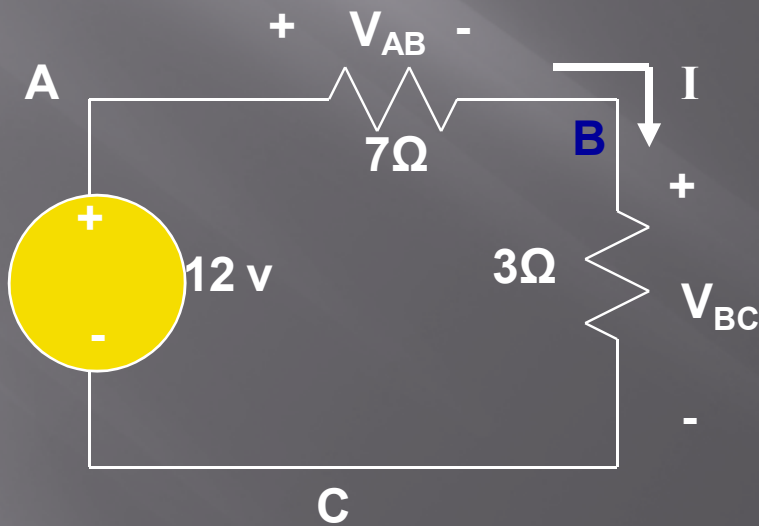So $V_{AB} = 8.4 \text{ v}$ and $V_{BC} = 3.6 \text{ v}$




Series Resistors

- 🌐 KVL: $+I \cdot 10\Omega - 12\text{ v} = 0$, So $I = 1.2\text{ A}$
- 🌐 From the viewpoint of the source, the 7 and 3 ohm resistors in series are equivalent to the 10 ohms



Series Resistors

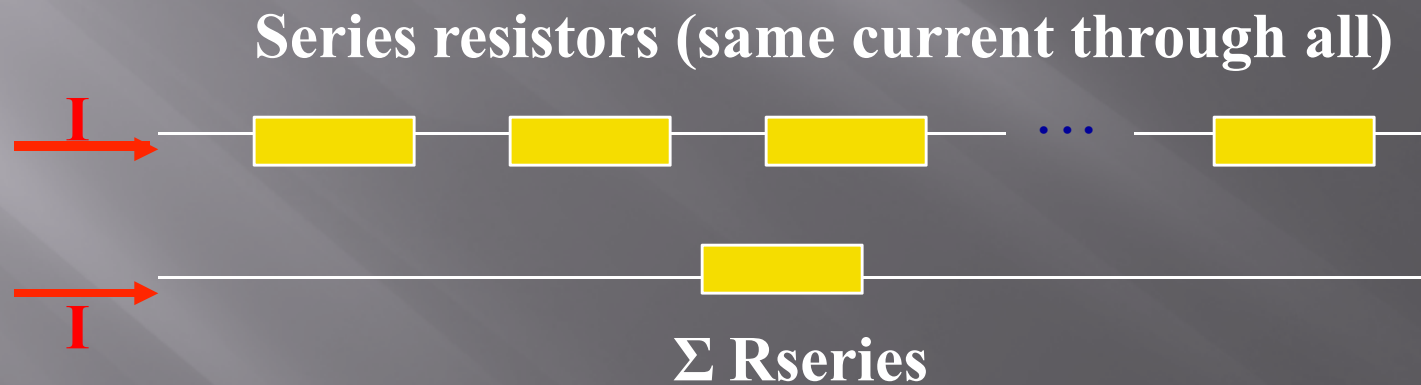- 🌐 To the rest of the circuit, series resistors can be replaced by an equivalent resistance equal to the sum of all resistors



Kirchoff's Current Law (KCL)

▣ The algebraic sum of currents entering a node is zero



The algebraic sum of currents entering a node is zero

▣ Add each branch current entering the node and subtract each branch current leaving the node



Add each branch current entering the node and subtract each branch current leaving the node


▣ Σ currents in - Σ currents out = 0 Or Σ

currents in = Σ currents out



Or Σ currents in = Σ currents out

Example

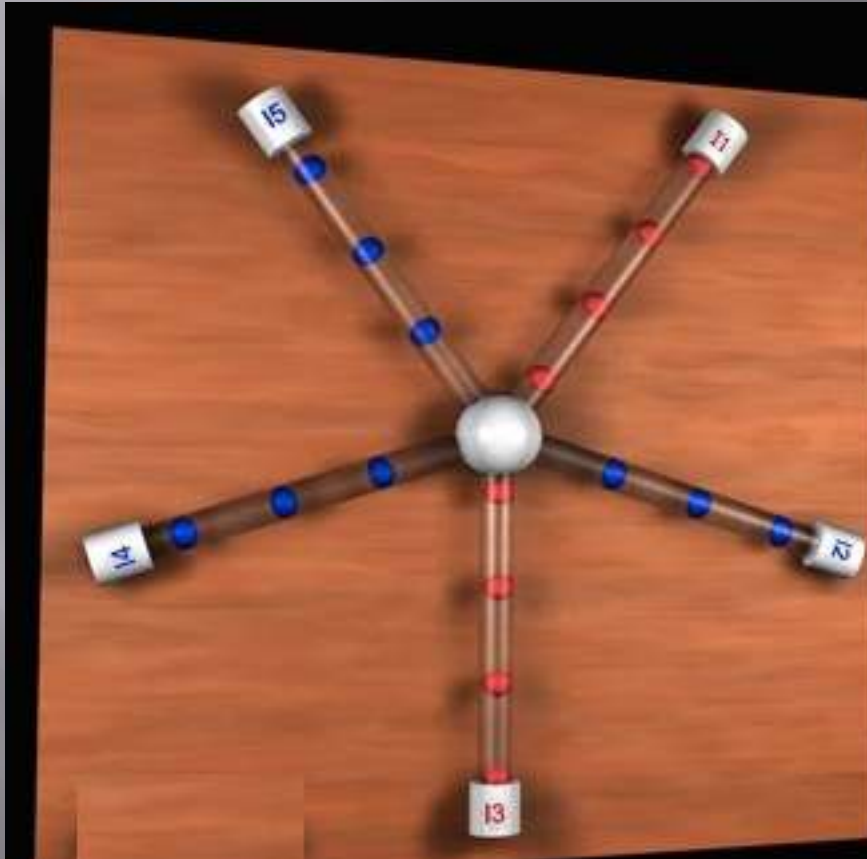


1º LEY DE KIRCHHOFF
Ley de los nodos

$$I_1 + I_3 = I_2 + I_4 + I_5$$

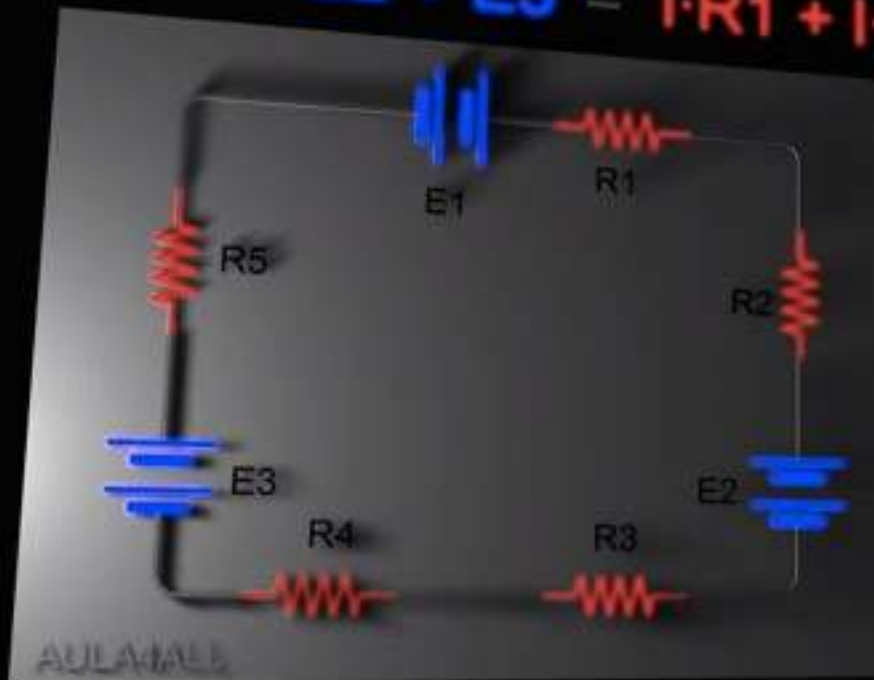Example

$$E1 - E2 + E3 = I \cdot R1 + I \cdot R2 + I \cdot R3 + I \cdot R4 + I \cdot R5$$




2º LEY DE KIRCHHOFF
Ley de las mallas

Example




Circuit Analysis

Circuit Analysis

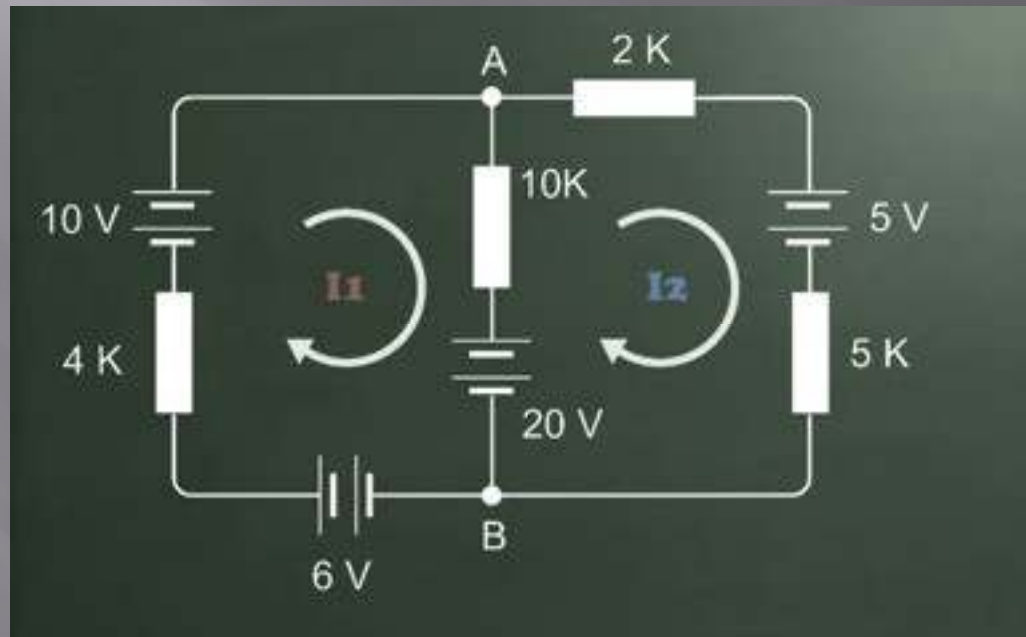


Circuit Analysis

Circuit Analysis

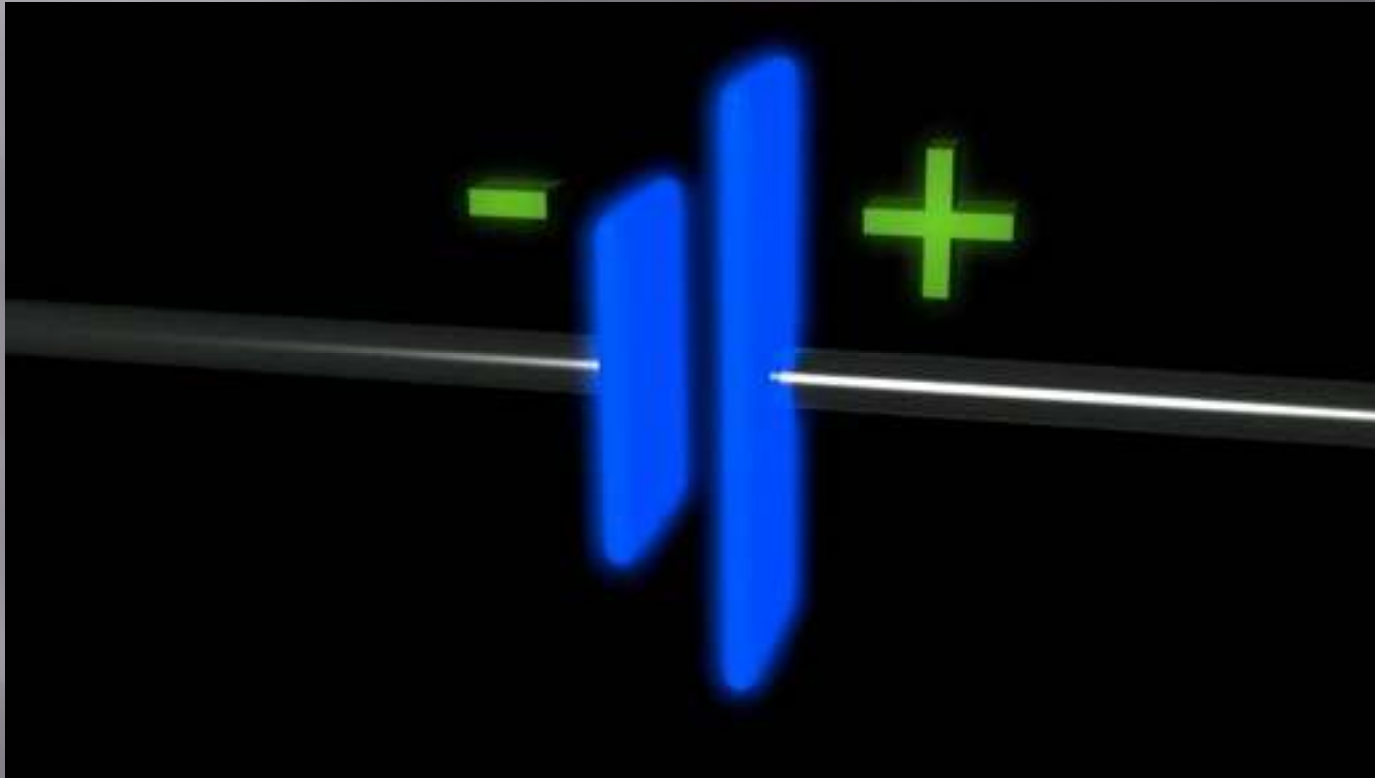

Circuit Analysis

Circuit Analysis

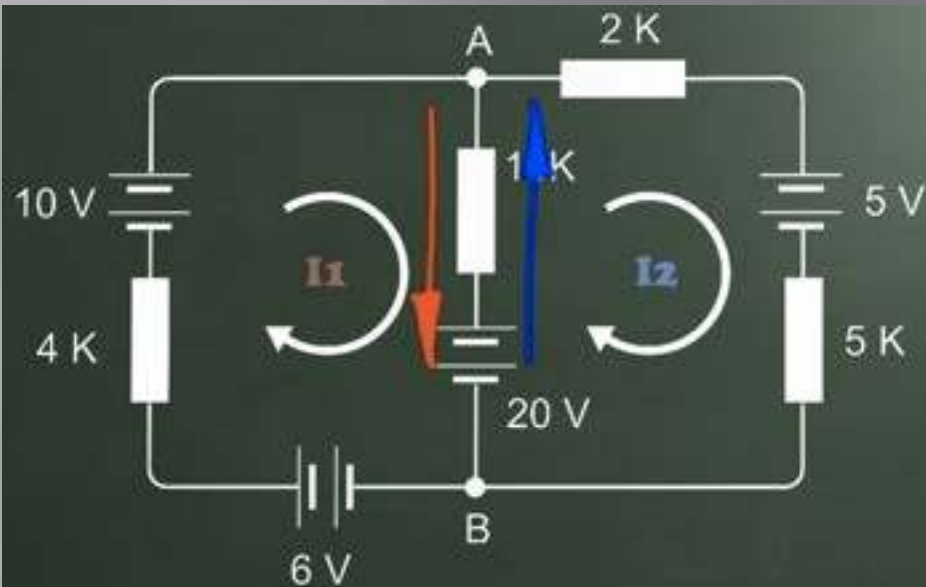

1ª Malla

$$10 - 20 + 6 = 4I_1 + 10(I_1 - I_2)$$

$$-4 = 4I_1 + 10I_1 - 10I_2$$

$$-4 = 14I_1 - 10I_2$$

2ª Malla

$$20 - 5 = 10(I_2 - I_1) + 2I_2 + 5I_2$$

$$15 = 10I_2 - 10I_1 + 2I_2 + 5I_2$$

$$-4 = 14I_1 - 10I_2$$

$$15 = -10I_1 + 17I_2$$

The second equation multiplied by 1.4

$$-4 = 14I_1 - 10I_2$$

$$21 = -14I_1 + 23,8I_2$$

$$-4 = 14I_1 - 10I_2$$

$$21 = -14I_1 + 23,8I_2$$

$$17 = 0 + 13,8I_2$$

$$I_2 = \frac{17}{13,8} = 1,23 \text{ mA.}$$

$$15 = 17I_2 - 10I_1$$

$$-4 = 14I_1 - 10(1,23)$$

$$-4 = 14I_1 - 12,3$$


$$-4 + 12,3 = 14I_1$$

$$8,3 = 14I_1$$

$$I_1 = 0,59 \text{ mA.}$$

Circuit Analysis

Circuit Analysis

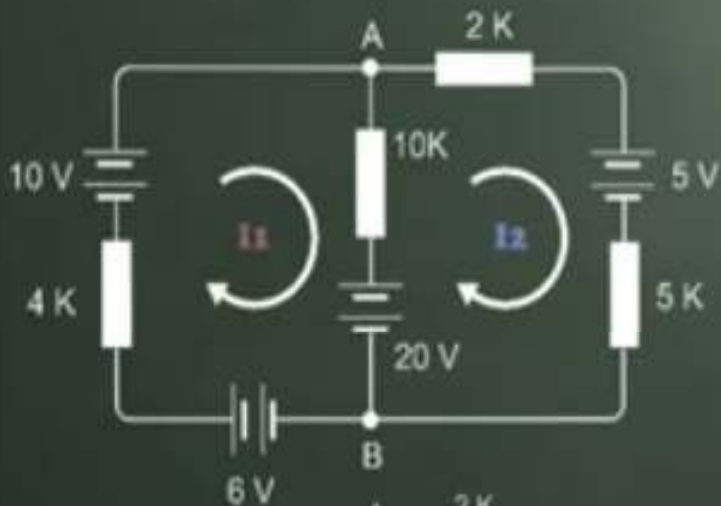

1º Malla

$$10 - 20 + 6 = 4I_1 + 10(I_1 - I_2)$$

$$-4 = 4I_1 + 10I_1 - 10I_2$$

$$-4 = 14I_1 - 10I_2$$

2º Malla

$$20 - 5 = 10(I_2 - I_1) + 2I_2 + 5I_2$$

$$15 = 10I_2 - 10I_1 + 2I_2 + 5I_2$$

$$15 = 17I_2 - 10I_1$$


RESOLVEMOS SISTEMA DE ECUACIONES

$$-4 = 14I_1 - 10I_2$$

$$21 = -14I_1 + 23,8I_2$$

$$17 = 0 + 13,8I_2$$
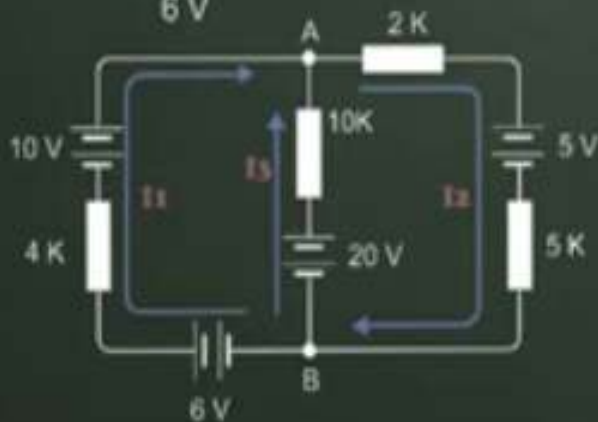
$$I_2 = \frac{17}{13,8} = 1,23 \text{ mA.}$$



$$I_2 = I_1 + I_3$$

$$I_3 = I_2 - I_1$$

$$I_3 = 1,23 - 0,59$$

$$I_3 = 0,6 \text{ mA.}$$

Sentido de I_3 va desde el nudo B al nudo A.

$$-4 = 14I_1 - 10(1,23)$$

$$-4 = 14I_1 - 12,3$$


$$-4 + 12,3 = 14I_1$$

$$8,3 = 14I_1$$

$$I_1 = 0,59 \text{ mA.}$$

Circuit Analysis

Circuit Analysis

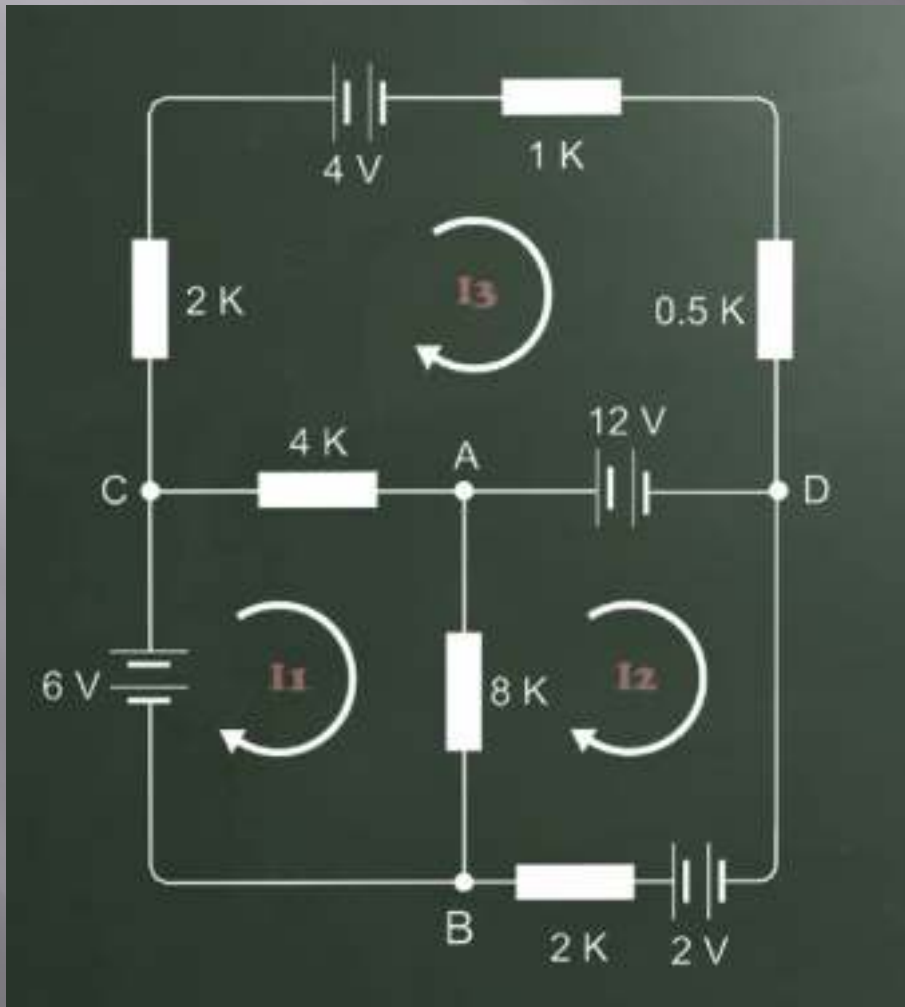

3ª Malla

$$12 - 4 = 4(I_3 - I_1) + 2I_3 + I_3 + 0,5 I_3$$

$$8 = 4I_3 - 4I_1 + 3,5I_3$$

$$8 = 7,5I_3 - 4I_1$$